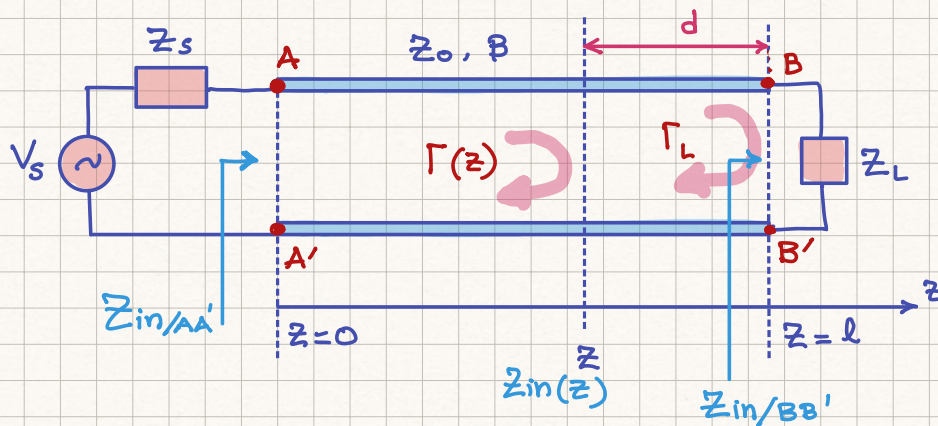


## A. IMPORTANT EQUATIONS OF IDEAL & LOSSLESS TRANSMISSION LINES



Assume  $f$  = frequency of source  
 $\lambda$  = wavelength

$$f \cdot \lambda = c \quad \omega = 2\pi f \quad \beta = \frac{2\pi}{\lambda}$$

$$\Gamma_L = \Gamma_{BB'} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_L = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)}$$

$$\Gamma_{AA'} = \frac{V_o^-}{V_o^+}$$

$$\Gamma(z) = \Gamma_L e^{-j2\beta d}$$

$$\Gamma(z) = \Gamma_{AA'} e^{j2\beta z}$$


$$Z_{in}(z) = \frac{V(z)}{I(z)}$$

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

$$\Gamma(z) = \frac{Z_{in}(z) - Z_0}{Z_{in}(z) + Z_0}$$


$$Z_{in}(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

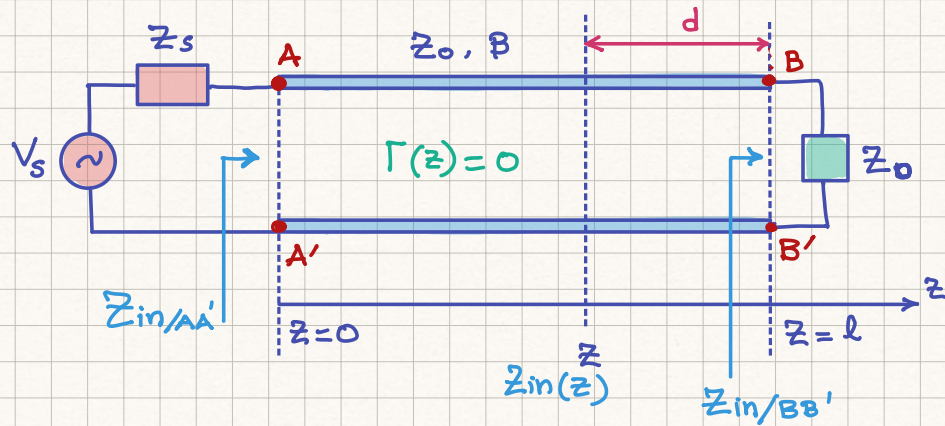B. **MATCHED LOSSLESS IDEAL**  
TRANSMISSION LINE ( $Z_L = Z_0$ )



$$\Gamma(z) = 0 \quad Z_{in}(z) = Z_0$$

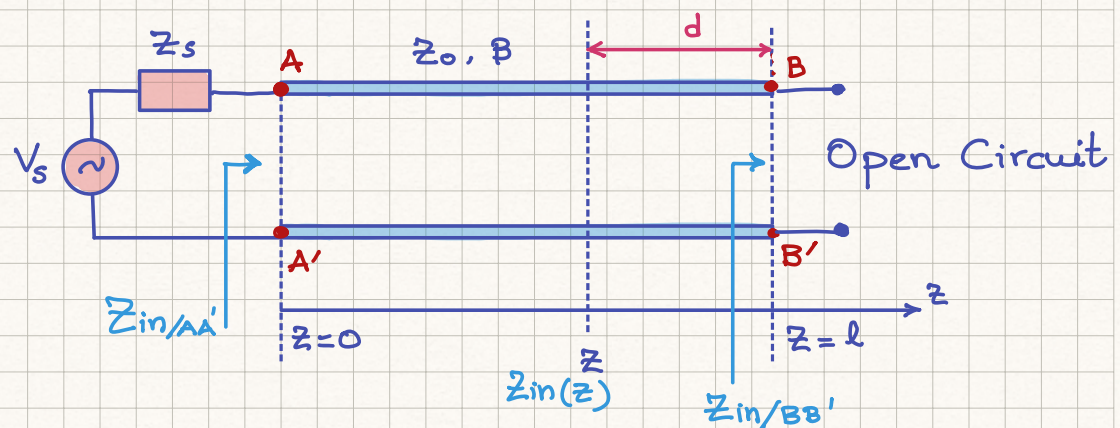C. **OPEN-ENDED IDEAL TRANSMISSION**  
LINE ( $Z_L = \infty$ )



at  $BB'$   $I_{BB'} = 0 \Rightarrow \frac{1}{Z_0} [V_o^+ e^{-j\beta l} - V_o^- e^{j\beta l}] = 0$

$$\Rightarrow V_o^+ = V_o^- e^{+j2\beta l}$$




$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 1 \Rightarrow$$

$$\Gamma_L = 1$$


$$\Gamma(z) = e^{-j2\beta d}$$

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

$$Z_{in}(z) = -jZ_0 \cot(\beta d)$$

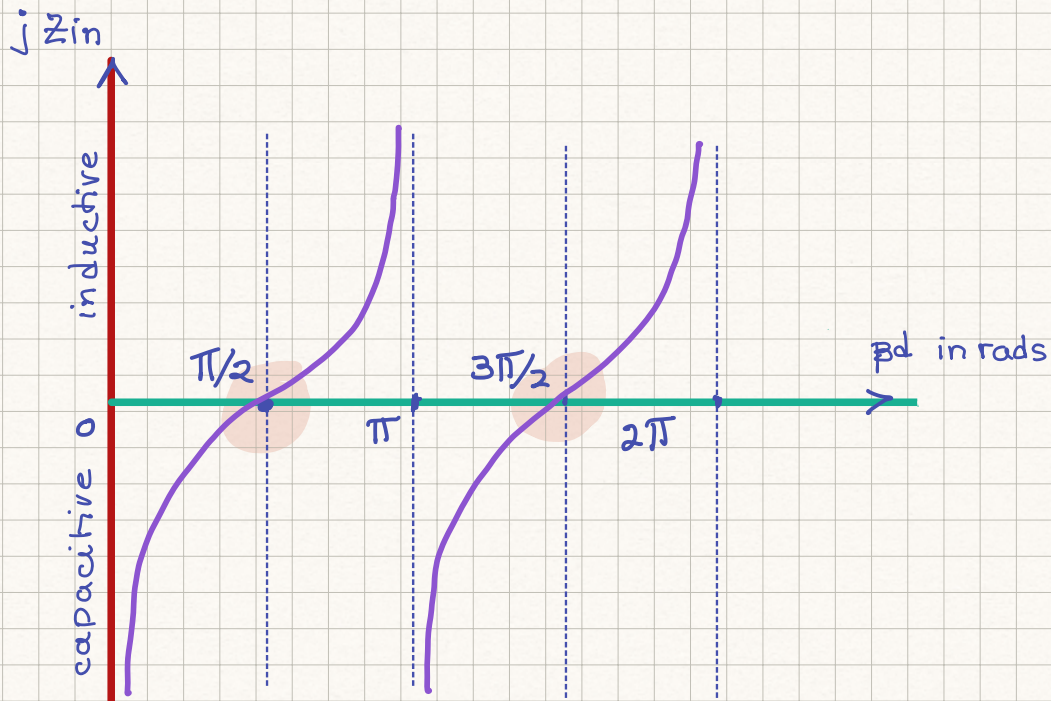

## SHORT-CIRCUIT IDEAL TRANSMISSION LINE

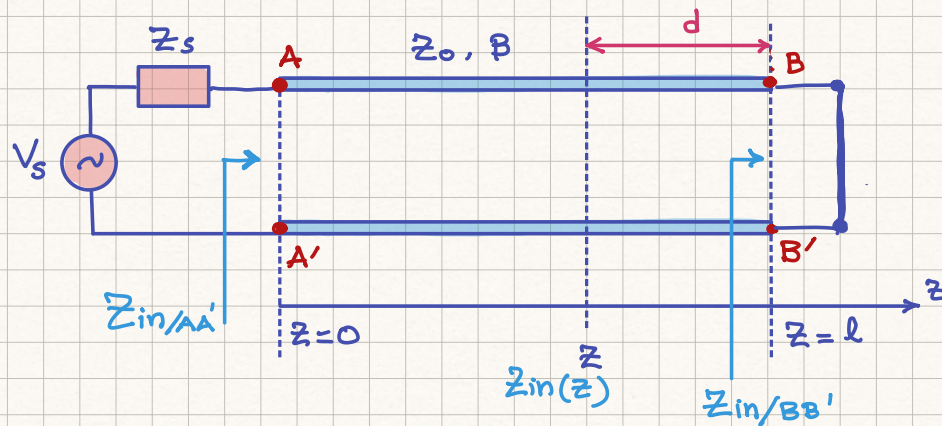

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \quad (Z_L = 0)$$

$$= Z_0 (j \tan(\beta d)) \Rightarrow$$

$$Z_{in}(z) = j Z_0 \tan(\beta d)$$

